Experimental Problem

Define the electrical circuit scheme in a “black box” and determine the parameters of its elements.

List of instruments: A DC source with tension 4.5 V, an AC source with 50 Hz frequency and output voltage up to 30 V, two multimeters for measuring AC/DC current and voltage, variable resistor, connection wires.